

$$R_1 = R_3 = R_4 = R_5 = 2 \Omega$$

$$R_2 = 4 \Omega$$

$$U_{e1} = 3V$$

$$U_{e2} = U_{e3} = 6V$$

$$I_1, I_2, I_3 = ?$$

$$I_1 + I_2 = I_3$$

$$R_1 I_1 + R_5 I_1 - R_2 I_2 = U_{e2} - U_{e1}$$

$$R_2 I_2 + R_4 I_3 + R_3 I_3 = U_{e3} - U_{e2}$$

$$\begin{aligned} I_1 + I_2 - I_3 &= 0 \quad / \cdot 4 \\ 4I_1 - 4I_2 &= 3 \\ 4I_2 + 4I_3 &= 0 \end{aligned}$$

$$8I_1 - 4I_3 = 3$$

$$4I_1 + 4I_3 = 3$$


$$12I_1 = 6$$

$$\underline{\underline{I_1 = \frac{1}{2} A}}$$

$$I_2 = \frac{4I_1 - 3}{4} = \underline{\underline{-\frac{1}{4} A}}$$

$$I_3 = I_1 + I_2 = \underline{\underline{\frac{1}{4} A}}$$

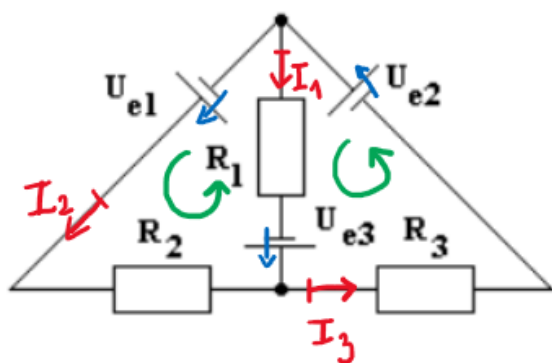$I_2 < 0 \Rightarrow$ má opačný směr, než jak je vyznačeno na obrázku



$$R_1 = 3\Omega$$

$$R_2 = 8\Omega$$

$$R_3 = 6\Omega$$

$$U_{e1} = 15V$$

$$U_{e2} = 12V$$

$$U_{e3} = 6V$$

$$\begin{aligned} I_1 + I_2 &= I_3 \\ -R_1 I_1 + R_2 I_2 &= U_{e1} - U_{e3} \\ R_1 I_1 + R_3 I_3 &= U_{e2} + U_{e3} \end{aligned}$$

$$\begin{aligned} I_1 + I_2 - I_3 &= 0 \quad | \cdot 6 \\ -3I_1 + 8I_2 &= 9 \\ 3I_1 + 6I_3 &= 18 \end{aligned}$$

$$\begin{aligned} 9I_1 + 6I_2 &= 18 \quad | : 3 \\ -3I_1 + 8I_2 &= 9 \end{aligned}$$

$$10I_2 = 15$$

$$\underline{\underline{I_2 = 1,5A}}$$

$$\begin{aligned} -3I_1 + 12 &= 9 \\ 3I_1 &= 3 \Rightarrow \underline{\underline{I_1 = 1A}} \end{aligned}$$

$$I_3 = I_1 + I_2 = 1 + 1,5 = \underline{\underline{2,5A}}$$